

RC circuits

- charging: When the capacitor is charging or storing electricity
- discharging: when the capacitor is losing electricity

Charging: Charge and Voltage rise and current decays

$$Q = C \mathcal{E} (1 - e^{-t/RC})$$

- Q = electric charge (C)
- \mathcal{E} = emf
- C = capacitor
- R = resistance

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$


- I = (charge (amps))
- \mathcal{E} = emf
- C = capacitor
- R = resistance

$$\Delta V(t) = \mathcal{E} (1 - e^{-t/RC})$$

- V = Voltage drop (V)
- \mathcal{E} = emf
- R = resistor
- C = capacitor


Q vs. T

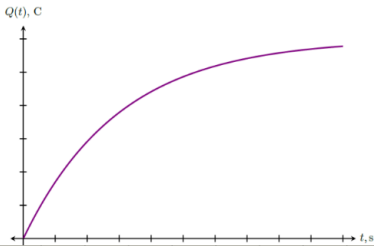The resulting plots look something like this:



I vs. T

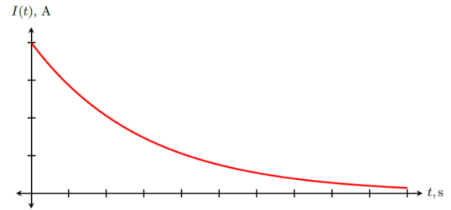The resulting plots look something like this:



• $\Delta V = \frac{Q}{C}$ you can apply this equation on charging or discharging its always true

✗ this only works For charging capacitors

When $T(\text{time})$ goes to infinite $\Delta V = \mathcal{E}$

$$\Delta V(\infty) = \mathcal{E} (1 - e^{-t/RC}) \Rightarrow \Delta V(\infty) = \mathcal{E} (1 - e^{-\frac{\infty}{RC}})$$

$$\Delta V = \mathcal{E}$$

• **discharging**: Charge and Voltage decay to zero

$$Q(t) = Q_0 e^{-t/RC}$$

$$Q_0 = C \mathcal{E}$$

Plug it in

$$Q(t) = C \mathcal{E} e^{-t/RC}$$

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$I(t) = \frac{Q_0}{\tau} e^{-t/\tau}$$

- I = current (amps)
- \mathcal{E} = emf
- R = resistance
- C = capacitor

$$\Delta V(t) = \mathcal{E} e^{-t/RC}$$

- ΔV = voltage drop (V)
- \mathcal{E} = emf
- R = resistance
- C = capacitor

• time constant and half life

$$\text{time constant} = \tau = RC \quad \text{half life} = t_{1/2} = \tau = \frac{t_{1/2}}{\ln(2)}$$


The half life helps you get the time constant once you get the half life ($t_{1/2}$) you can solve for the time constant

★ You can use the half life equation on a discharging graph or a charging capacitor graph

how to get the half life:

Q vs. T

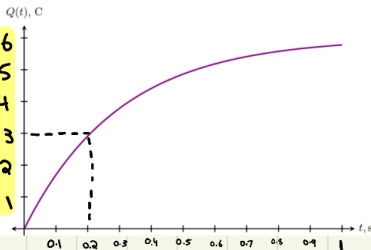The resulting plots look something like this:



take the charge and divide it by 2

$$6Q/2 = 3$$

now go to three ($3Q$) and see where the the graph will cross or the time at the point is

so the half life ($t_{1/2} = 0.2$) Now plug that into:

$$\tau = \frac{t_{1/2}}{\ln(2)}$$

• Capacitor in circuits

• Capacitor in Series


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

★ Capacitors in Series have the Same Charge Q

• Capacitors in Series

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$

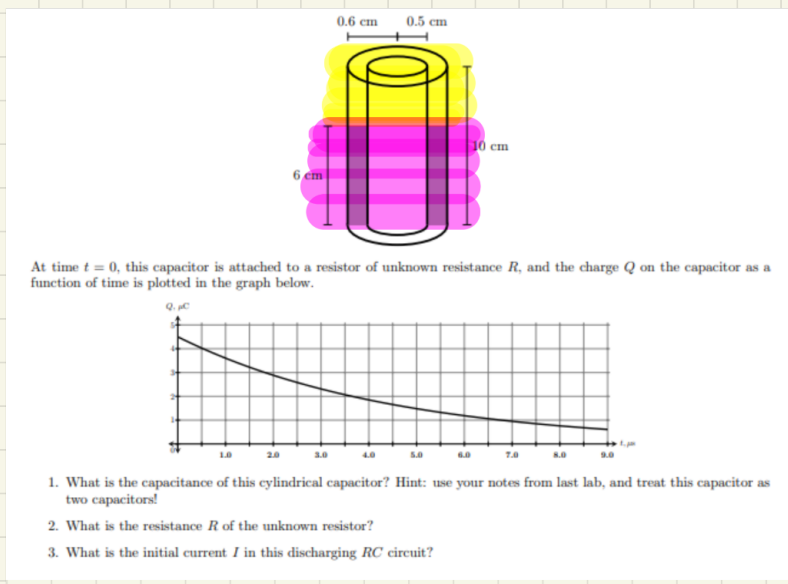★ Capacitors in Parallel have the Same Voltage V



the best way to solve is to break it in two parts into this part and the second part you will use this equation:

$$C = \frac{2\pi L \epsilon_0}{\ln(b/a)} \quad \text{and} \quad C = \frac{2\pi L K \epsilon_0}{\ln(b/a)}$$

as the second part has dielectric

★ you can add capacitors together

$$C = \frac{2\pi (0.04) (8.85 \times 10^{-12})}{\ln\left(\frac{0.006}{0.005}\right)} + \frac{2\pi (0.06) (20.7) (8.85 \times 10^{-12})}{\ln\left(\frac{0.006}{0.005}\right)} = \boxed{3.79 \times 10^{-10} \text{ F}}$$

to Find R we will use half life

$$\textcircled{2} \quad t_{1/2} = \frac{4.5}{2} = 2.25 \mu\text{s} = 3.0 \times 10^{-6}$$

$$\gamma = \frac{t_{1/2}}{\ln(2)} = \frac{3.0 \times 10^{-6}}{\ln(2)} = 4.32 \times 10^{-6} \text{ s}$$

$$\gamma = RC$$

$$4.32 \times 10^{-6} = R (3.79 \times 10^{-10})$$

$$\boxed{R = 11419 \Omega}$$

$\textcircled{3}$

$$I(t) = \frac{Q_0}{\gamma} e^{-t/\gamma} = \frac{4.5 \times 10^{-6}}{4.47 \times 10^{-6}} \cdot e^{-0/4.47 \times 10^{-6}} = \boxed{1.0 \text{ A}}$$